

# Lab 10: Vending Machine

**Due: May 14, 2015**

---

## Objective

- To be familiar with modeling finite state machines with Verilog.

## Action Items

1. Design a controller for a soft drink vending machine. The controller has the following input ports:

```
input clk;  
input rst_n;  
input cancel;  
input tea;  
input coke;  
input sprite;  
input money_5;  
input money_10;  
input money_50;
```

and the following output ports:

```
output drop_tea;  
output drop_coke;  
output drop_sprite;  
output [3:0] DIGIT;  
output [7:0] DISPLAY;
```

- When pressing the rst\_n button, the two leftmost 7-segment displays will show "00", and the two rightmost 7-segment displays will show nothing. The three LEDs respectively corresponding to drop\_tea, drop\_coke and drop\_sprite will not light up.
- Every time after a buyer deposits a coin (NT\$ 5, 10, or 50), the two leftmost 7-segment displays will immediately show the total amount of money that has been deposited so far. If a buyer wants

to deposit NT\$ 5, he/she presses the money\_5 button; if a buyer wants to deposit NT\$ 10, he/she presses the money\_10 button; if a buyer wants to deposit NT\$ 50, he/she presses the money\_50 button.

- A buyer may deposit any number of coins. If the buyer deposits more than NT\$ 50, treat it as NT\$ 50.
- Each bottle of tea costs NT\$ 15, each bottle of coke costs NT\$ 20 and each can of sprite costs NT\$ 25. If the deposited money is not enough, then pushing the tea, coke or sprite button does not effect, and the LED corresponding to the drop\_tea, drop\_coke or drop\_sprite will not light up.
- When the money deposited so far is enough for buying a drink, the LED corresponding to drop\_tea, drop\_coke or drop\_sprite will light up. After the buyer selects tea, coke or sprite by pushing the corresponding button, the two leftmost 7-segment displays will show the change to be returned to the buyer, where the change will be decremented by NT\$ 5 (to simulate dropping a coin of NT\$ 5) at each clock cycle (**with the frequency of  $\text{clk}/(2^{25})$** ) until 00 is reached. After the change becomes 00, the buyer can deposit coins again. The buyer cannot buy another drink while the machine is returning the change.
- If the buyer decides not to buy any drink (no matter how much money has been deposited), he/she can press the cancel button for getting the money back (but at most NT\$ 50 will be returned if more than NT\$ 50 have been deposited). The money will be returned in the same way as returning the change.

More details about the I/O signals of the design are given below.

- **clk**: clock signal (which is connected to the FPGA pin **R10**).
- **rst\_n**: asynchronous negative trigger reset which is generated from an onepulse circuit whose input comes from the output of a debouncer; the data input of the debouncer is the pushbutton **S1** connected to the FPGA pin **N3**. When rst\_n is enabled, the numbers being shown on the two leftmost 7-segment displays are set to 0.
- **cancel**: the cancel button which is generated from an onepulse

circuit whose input comes from the output of a debouncer; the data input of the debouncer is the pushbutton **S8** connected to the FPGA pin **T2**.

- **tea**: the tea button which is generated from an onepulse circuit whose input comes from the output of a debouncer; the data input of the debouncer is the pushbutton **S2** connected to the FPGA pin **P4**.
- **coke**: the coke button which is generated from an onepulse circuit whose input comes from the output of a debouncer; the data input of the debouncer is the pushbutton **S3** connected to the FPGA pin **P3**.
- **sprite**: the sprite button which is generated from an onepulse circuit whose input comes from the output of a debouncer; the data input of the debouncer is the pushbutton **S4** connected to the FPGA pin **L6**.
- **money\_5**: the money\_5 button which is generated from a onepulse circuit whose input comes from the output of a debouncer; the data input of the debouncer is the pushbutton **S5** connected to the FPGA pin **M5**.
- **money\_10**: the money\_10 button which is generated from a onepulse circuit whose input comes from the output of a debouncer; the data input of the debouncer is the pushbutton **S6** connected to the FPGA pin **U2**.
- **money\_50**: the money\_50 button which is generated from a onepulse circuit whose input comes from the output of a debouncer; the data input of the debouncer is the pushbutton **S7** connected to the FPGA pin **U1**.
- **DISPLAY**: signal to show the money that has been deposited so far, or the money to be returned.
- **DIGIT**: signal to enable one 7-segment display.
- **drop\_tea**: the drop\_tea signal which is the LED **D1** connected to the FPGA pin **K4**.
- **drop\_coke**: the drop\_coke signal which is the LED **D2** connected to the FPGA pin **K3**.
- **drop\_sprite**: the drop\_sprite signal which is the LED **D3** connected to the FPGA pin **L5**.

2. Before you add the debouncing and one-pulse circuits to your design, write a testbench, including at least the following input stimuli, to verify your controller.
  - a. Deposits NT\$ 15 ( $\text{NT\$ } 5 + \text{NT\$ } 10$ ) and selects tea.
  - b. Deposits NT\$ 20 ( $2 * \text{NT\$ } 5 + \text{NT\$ } 10$ ) and selects coke.
  - c. Deposits NT\$ 60 ( $\text{NT\$ } 10 + \text{NT\$ } 50$ ) and selects sprite.
  - d. Deposits NT\$ 100 ( $2 * \text{NT\$ } 5 + 4 * \text{NT\$ } 10 + \text{NT\$ } 50$ ) and selects cancel.